



Nodal Analysis: method to solve a circuit by finding all nodal voltages.

How?

(Pick largest node)


- 1) Define one node as GROUND in case circuit doesn't have ground defined.
- 2) Label all other nodes
- 3) For voltage supplies:
  - a. if supply is connected to ground, that node is defined by it  
→ SKIP STEP 4 on the nodes that are defined
  - b. if supply is between two nodes that are NOT defined, then we say this is a SUPERNODE and we write a SUPERNODE expression relating the two nodes. We also use Step 4 for Supernodes.
- 4) write KCL expressions for all labeled (super)nodes that are undefined
- 5) write Ohm's laws for all currents as functions of nodal voltages.
- 6) write a system of equations with  $x$  variables, where  $x = \# \text{ nodes} - \# \text{ V supplies} - 1$   
 $\uparrow$   $\uparrow$   $\uparrow$   
 $\# \text{ of KCL equations}$   $\# \text{ of ground}$

Ex: Solve using NA:

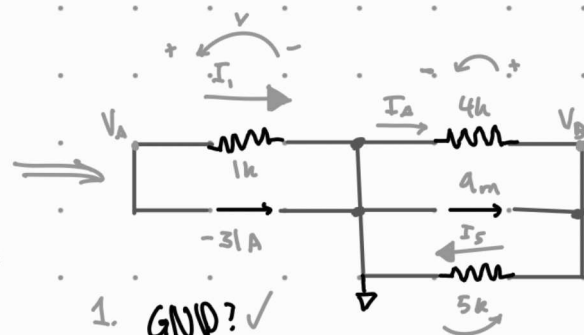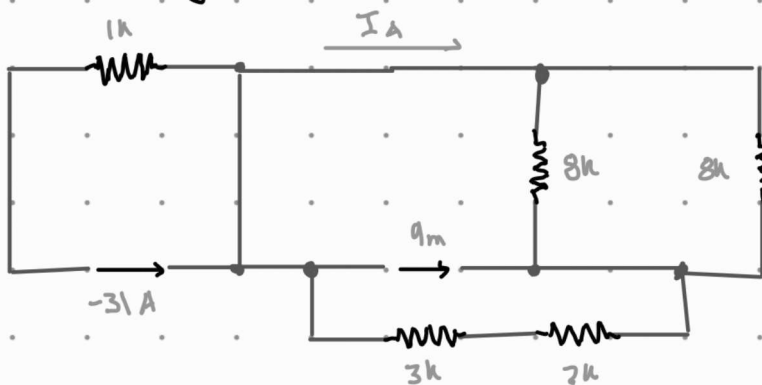

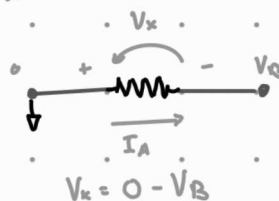1. GND? ✓
2.  $V_A, V_B$
4. KCL: ( $V_A$ ):  $0 = I_1 + (-3I_A)$   
 ( $V_B$ ):  $I_A + 9m = I_5$

$$\begin{aligned}
 5. \quad I_1 &= V_A / 1k \\
 I_A &= -V_B / 4k \\
 I_5 &= V_B / 5k
 \end{aligned}$$



$$6. \quad \# \text{ of KCL} = \# \text{ nodes} - \# \text{ V supplies} - 1 \rightarrow 2 = 3 - 0 - 1$$

$$\frac{V_A}{1k} = \frac{3(-V_B)}{4k} \rightarrow 4V_A = -3V_B \rightarrow 4V_A + 3V_B = 0$$

Wrong

$$\frac{V_B}{1k} + 9m = \frac{V_B}{5k} \rightarrow 5V_A + 45 = V_B \rightarrow 5V_A - V_B = -45$$

Exam Answer:

$$\begin{bmatrix} 4 & 3 \\ 5 & -1 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ -45 \end{bmatrix}$$